

Ejemplos resueltos de Potencia compleja

➤ **EXAMPLE 17-2** For the RL circuit of Figure 17-7(a), $I = 5$ A. Determine P and Q .

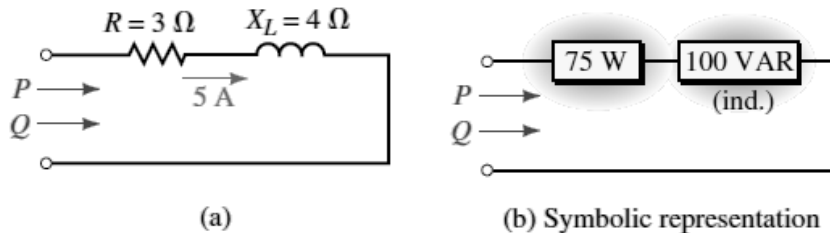


FIGURE 17-7 From the terminals, P and Q are the same for both (a) and (b).

Solution

$$P = I^2 R = (5\text{ A})^2 (3\ \Omega) = 75\text{ W}$$

$$Q = Q_L = I^2 X_L = (5\text{ A})^2 (4\ \Omega) = 100\text{ VAR (ind.)}$$

These can be represented symbolically as in Figure 17-7(b).

➤ **EXAMPLE 17-3** For the RC circuit of Figure 17-8(a), determine P and Q .

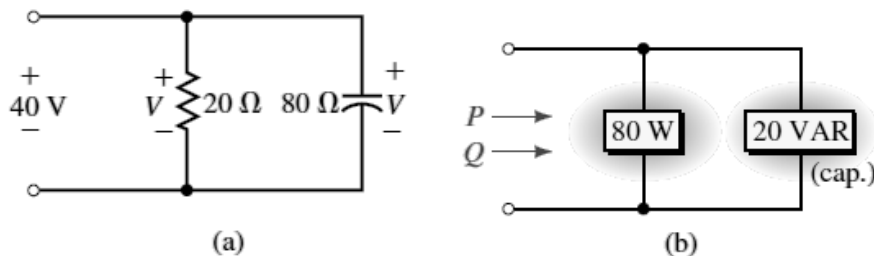


FIGURE 17-8 From the terminals, P and Q are the same for both (a) and (b).

Solution


$$P = V^2/R = (40\text{ V})^2/(20\ \Omega) = 80\text{ W}$$

$$Q = Q_C = V^2/X_C = (40\text{ V})^2/(80\ \Omega) = 20\text{ VAR (cap.)}$$


These can be represented symbolically as in Figure 17-8(b).

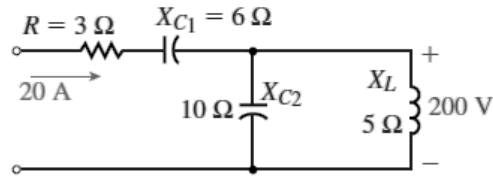EXAMPLE 17-4

- For Figure 17-9(a), compute P_T and Q_T .
- Reduce the circuit to its simplest form.




(a)

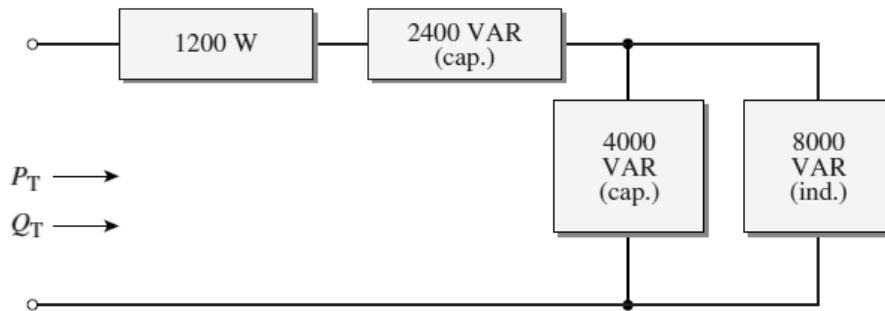


(b)

FIGURE 17-9

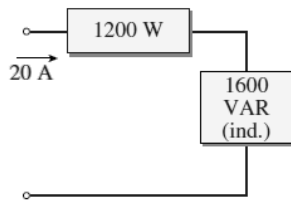

(c)

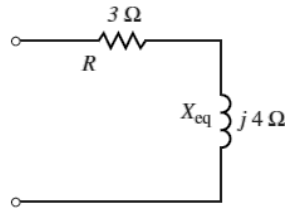

(d)

FIGURE 17-9 Continued.

Solution

- $P = I^2 R = (20 \text{ A})^2 (3 \Omega) = 1200 \text{ W}$
 $Q_{C1} = I^2 X_{C1} = (20 \text{ A})^2 (6 \Omega) = 2400 \text{ VAR (cap.)}$
 $Q_{C2} = \frac{V_2^2}{X_{C2}} = \frac{(200 \text{ V})^2}{(10 \Omega)} = 4000 \text{ VAR (cap.)}$
 $Q_L = \frac{V_2^2}{X_L} = \frac{(200 \text{ V})^2}{5 \Omega} = 8000 \text{ VAR (ind.)}$

These are represented symbolically in part (b). $P_T = 1200 \text{ W}$ and $Q_T = -2400 \text{ VAR} - 4000 \text{ VAR} + 8000 \text{ VAR} = 1600 \text{ VAR}$. Thus, the load is net inductive as shown in (c).

- $Q_T = I^2 X_{eq}$. Thus, $X_{eq} = Q_T / I^2 = (1600 \text{ VAR}) / (20 \text{ A})^2 = 4 \Omega$. Circuit resistance remains unchanged. Thus, the equivalent is as shown in (d).

EXAMPLE 17-7 For the circuit of Figure 17-18(b), a capacitance with $Q_C = 160 \text{ kVAR}$ is added in parallel with the load as in Figure 17-19(a). Determine generator current I .

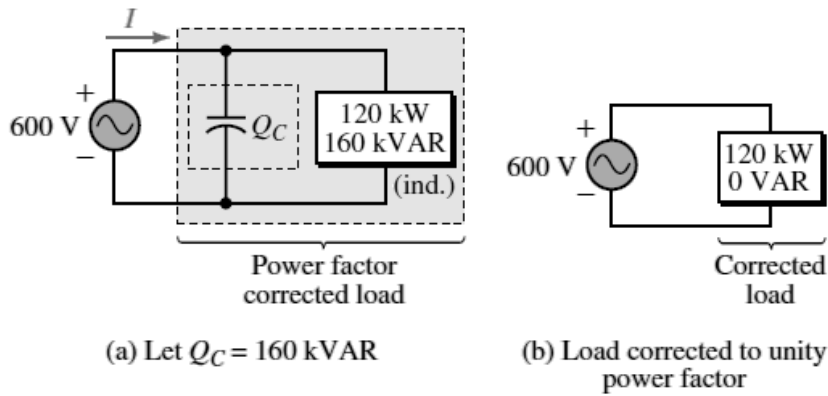


FIGURE 17-19 Power factor correction. The parallel capacitor greatly reduces source current.

Solution $Q_T = 160 \text{ kVAR} - 160 \text{ kVAR} = 0$. Therefore, $S_T = 120 \text{ kW} + j0 \text{ kVAR}$. Thus, $S_T = 120 \text{ kVA}$, and $I = 120 \text{ kVA}/600 \text{ V} = 200 \text{ A}$. Thus, the generator is no longer overloaded.

EXAMPLE 17-8 An industrial client is charged a penalty if the plant power factor drops below 0.85. The equivalent plant loads are as shown in Figure 17-20. The frequency is 60 Hz.

- Determine P_T and Q_T .
- Determine what value of capacitance (in microfarads) is required to bring the power factor up to 0.85.
- Determine generator current before and after correction.

Solution

- The components of power are as follows:

Lights: $P = 12 \text{ kW}$, $Q = 0 \text{ kVAR}$

Furnace: $P = I^2 R = (150)^2(2.4) = 54 \text{ kW}$

$Q = I^2 X = (150)^2(3.2) = 72 \text{ kVAR (ind.)}$

Motor: $\theta_m = \cos^{-1}(0.8) = 36.9^\circ$. Thus, from the motor power triangle,

$Q_m = P_m \tan \theta_m = 80 \tan 36.9^\circ = 60 \text{ kVAR (ind.)}$

Total: $P_T = 12 \text{ kW} + 54 \text{ kW} + 80 \text{ kW} = 146 \text{ kW}$

$Q_T = 0 + 72 \text{ kVAR} + 60 \text{ kVAR} = 132 \text{ kVAR}$

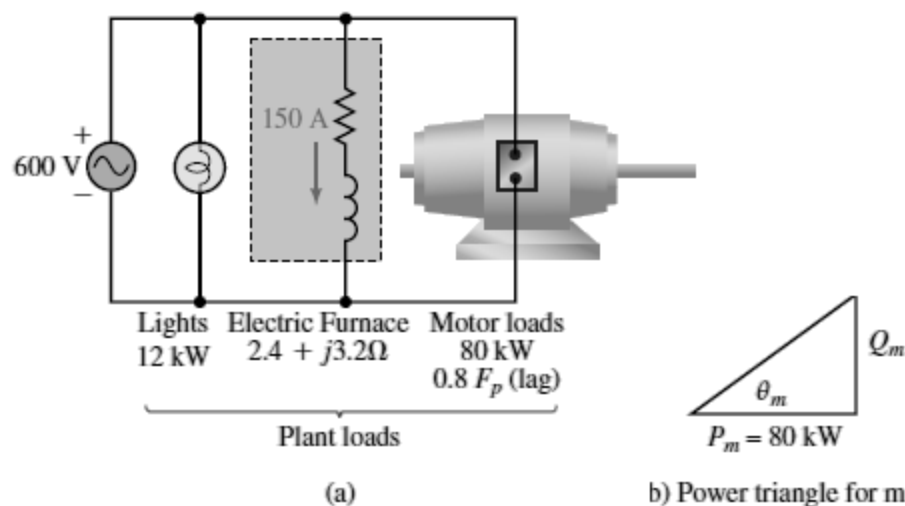


FIGURE 17-20

- b. The power triangle for the plant is shown in Figure 17-21(a). However, we must correct the power factor to 0.85. Thus we need $\theta' = \cos^{-1}(0.85) = 31.8^\circ$, where θ' is the power factor angle of the corrected load as indicated in Figure 17-21(b). The maximum reactive power that we can tolerate is thus $Q'_T = P_T \tan \theta' = 146 \tan 31.8^\circ = 90.5 \text{ kVAR}$.

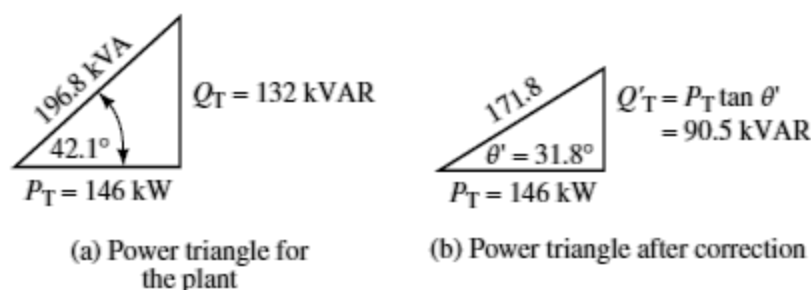


FIGURE 17-21 Initial and final power triangles. Note that P_T does not change when we correct the power factor.

Now consider Figure 17-22. $Q'_T = Q_C + 132 \text{ kVAR}$, where $Q'_T = 90.5 \text{ kVAR}$. Therefore, $Q_C = -41.5 \text{ kVAR} = 41.5 \text{ kVAR (cap.)}$. But $Q_C = V^2/X_C$. Therefore, $X_C = V^2/Q_C = (600)^2/41.5 \text{ kVAR} = 8.67 \Omega$. But $X_C = 1/\omega C$. Thus a capacitor of

$$C = \frac{1}{\omega X_C} = \frac{1}{(2\pi)(60)(8.67)} = 306 \mu\text{F}$$

will provide the required correction.

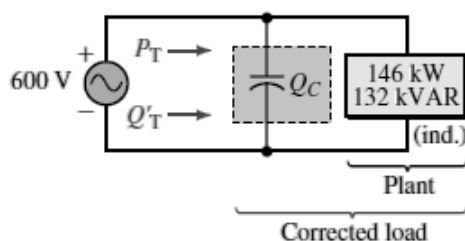


FIGURE 17-22

- c. For the original circuit Figure 17-21(a), $S_T = 196.8 \text{ kVA}$. Thus,

$$I = \frac{S_T}{E} = \frac{196.8 \text{ kVA}}{600 \text{ V}} = 328 \text{ A}$$

For the corrected circuit 17-21(b), $S'_T = 171.8 \text{ kVA}$ and

$$I = \frac{171.8 \text{ kVA}}{600 \text{ V}} = 286 \text{ A}$$

Thus, power factor correction has dropped the current by 42 A.