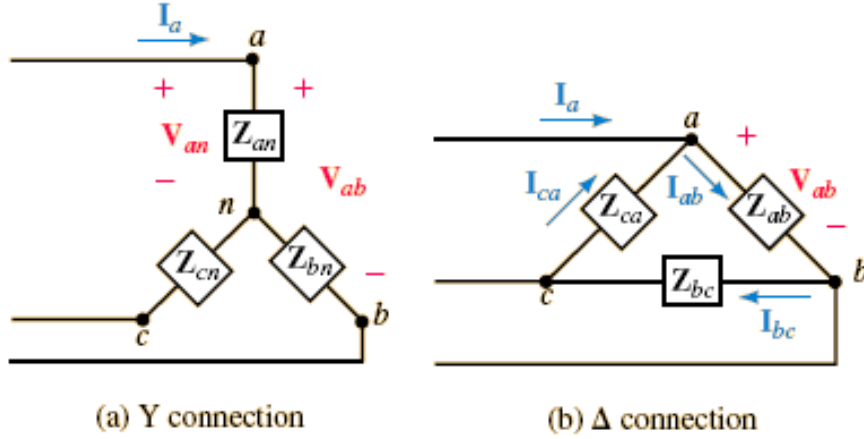


## Algunos ejemplos resueltos

### Para un sistema balanceado (resumen)



$$V_{ab} = \sqrt{3}V_{an}\angle 30^\circ$$

$$I_a = V_{an}/Z_{an}$$

$$Z_{an} = Z_{bn} = Z_{cn}$$

$$I_a = \sqrt{3}I_{ab}\angle -30^\circ$$

$$I_{ab} = V_{ab}/Z_{ab}$$

$$Z_{ab} = Z_{bc} = Z_{ca}$$

$$\text{Generator } E_{AB} = \sqrt{3}E_{AN}\angle 30^\circ$$

#### Active Power to a Balanced Wye Load

First, consider a Y load (Figure 23–22). The power to any phase as indicated in (b) is the product of the magnitude of the phase voltage  $V_\phi$  times the magnitude of the phase current  $I_\phi$  times the cosine of the angle  $\theta_\phi$  between them. Since the angle between voltage and current is always the angle of the load impedance, the power per phase is

$$P_\phi = V_\phi I_\phi \cos \theta_\phi \quad (\text{W}) \quad (23-10)$$

where  $\theta_\phi$  is the angle of  $Z_\phi$ . Total power is

$$P_T = 3P_\phi = 3V_\phi I_\phi \cos \theta_\phi \quad (\text{W}) \quad (23-11)$$

It is also handy to have a formula for power in terms of line quantities. For a Y load,  $I_\phi = I_L$  and  $V_\phi = V_L/\sqrt{3}$ , where  $I_L$  is the magnitude of the line current and  $V_L$  is the magnitude of the line-to-line voltage. Substituting these relations into Equation 23–11 and noting that  $3/\sqrt{3} = \sqrt{3}$  yields

$$P_T = \sqrt{3}V_L I_L \cos \theta_\phi \quad (\text{W}) \quad (23-12)$$


This is a very important formula and one that is widely used. Note carefully, however, that  $\theta_\phi$  is the angle of the load impedance and not the angle between  $V_L$  and  $I_L$ .

Power per phase can also be expressed as


$$P_\phi = I_\phi^2 R_\phi = V_R^2 / R_\phi \quad (\text{W}) \quad (23-13)$$

where  $R_\phi$  is the resistive component of the phase impedance and  $V_R$  is the voltage across it. Total power is thus
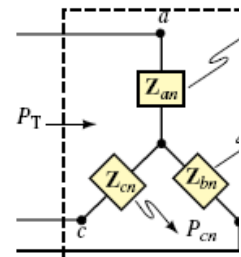
$$P_T = 3I_\phi^2 R_\phi = 3V_R^2 / R_\phi \quad (\text{W}) \quad (23-14)$$



(a)  $P_T = P_{an} + P_{bn} + P_{cn}$

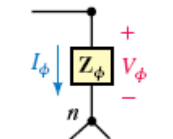

(b)

**FIGURE 23–22** For a balanced Y load,  $P_\phi = P_{an} = P_{bn} = P_{cn}$ .

### Reactive Power to a Balanced Wye Load

Equivalent expressions for reactive power are

$$Q_\phi = V_\phi I_\phi \sin \theta_\phi \quad (\text{VAR}) \quad (23-15)$$

$$= I_\phi^2 X_\phi = V_x^2 / X_\phi \quad (\text{VAR}) \quad (23-16)$$

$$Q_T = \sqrt{3} V_L I_L \sin \theta_\phi \quad (\text{VAR}) \quad (23-17)$$

where  $X_\phi$  is the reactive component of  $Z_\phi$  and  $V_x$  is the voltage across it.


### Apparent Power

$$S_\phi = V_\phi I_\phi = I_\phi^2 Z_\phi = \frac{V_\phi^2}{Z_\phi} \quad (\text{VA}) \quad (23-18)$$


$$S_T = \sqrt{3} V_L I_L \quad (\text{VA}) \quad (23-19)$$
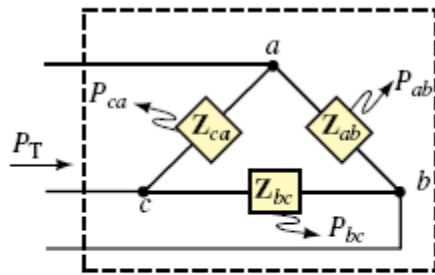
### Power Factor

$$F_p = \cos \theta_\phi = P_T / S_T = P_\phi / S_\phi \quad (23-20)$$



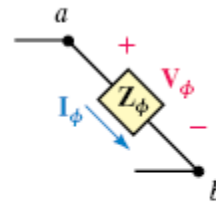(a)  $P_T = P_{ab} + P_{bc} + P_{ca} = 3 P_\phi$ .





(b)  $P_\phi = V_\phi I_\phi \cos \theta_\phi$   
 $\theta_\phi$  is angle of load impedance

**FIGURE 23-24** For a balanced  $\Delta$ ,  $P_\phi = P_{ab} = P_{bc} = P_{ca}$ .

Active power	$P_\phi = V_\phi I_\phi \cos \theta_\phi = I_\phi^2 R_\phi = \frac{V_R^2}{R_\phi}$ $P_T = \sqrt{3} V_L I_L \cos \theta_\phi$
Reactive power	$Q_\phi = V_\phi I_\phi \sin \theta_\phi = I_\phi^2 X_\phi = \frac{V_x^2}{X_\phi}$ $Q_T = \sqrt{3} V_L I_L \sin \theta_\phi$
Apparent power	$S_\phi = V_\phi I_\phi = I_\phi^2 Z_\phi = \frac{V_\phi^2}{Z_\phi}$ $S_T = \sqrt{3} V_L I_L$
Power factor	$F_p = \cos \theta_\phi = \frac{P_T}{S_T} = \frac{P_\phi}{S_\phi}$
Power triangle	$S_T = P_T + jQ_T$

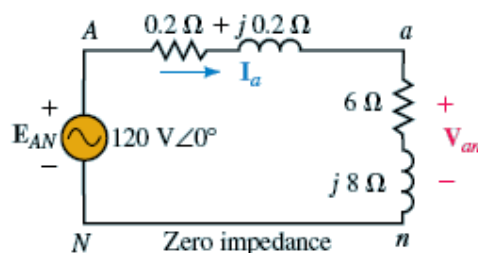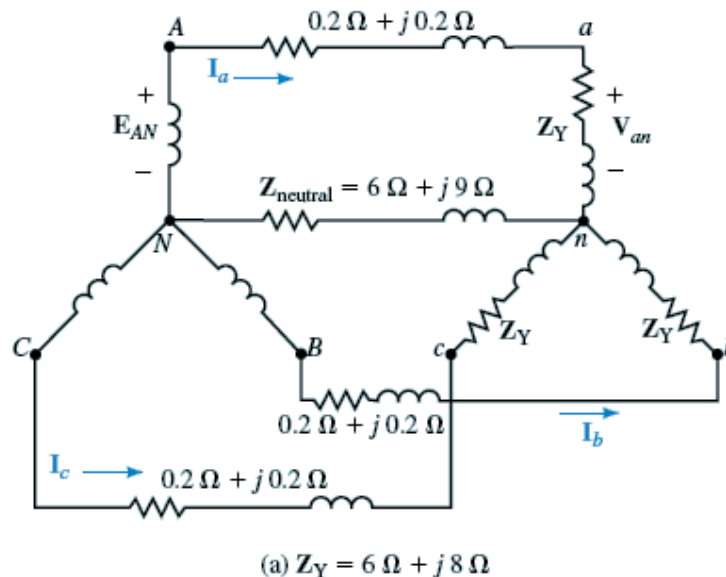**EXAMPLE 23-6** For Figure 23-16,  $E_{AN} = 120 \text{ V} \angle 0^\circ$ .

- Solve for the line currents.
- Solve for the phase voltages at the load.
- Solve for the line voltages at the load.



### Solution

- Reduce the circuit to its single-phase equivalent as shown in (b).

$$I_a = \frac{E_{AN}}{Z_T} = \frac{120 \angle 0^\circ}{(0.2 + j0.2) + (6 + j8)} = 11.7 \text{ A} \angle -52.9^\circ$$

Therefore,

$$I_b = 11.7 \text{ A} \angle -172.9^\circ \quad \text{and} \quad I_c = 11.7 \text{ A} \angle 67.1^\circ$$

- $V_{an} = I_a \times Z_{an} = (11.7 \angle -52.9^\circ)(6 + j8) = 117 \text{ V} \angle 0.23^\circ$

Thus,

$$V_{bn} = 117 \text{ V} \angle -119.77^\circ \quad \text{and} \quad V_{cn} = 117 \text{ V} \angle 120.23^\circ$$

- $V_{ab} = \sqrt{3} V_{an} \angle 30^\circ = \sqrt{3} \times 117 \angle (0.23^\circ + 30^\circ) = 202.6 \text{ V} \angle 30.23^\circ$


Thus,

$$V_{bc} = 202.6 \text{ V} \angle -89.77^\circ \quad \text{and} \quad V_{ca} = 202.6 \text{ V} \angle 150.23^\circ$$

Note the phase shift and voltage drop across the line impedance. Note also that the impedance of the neutral conductor plays no part in the solution, since no current passes through it because the system is balanced.

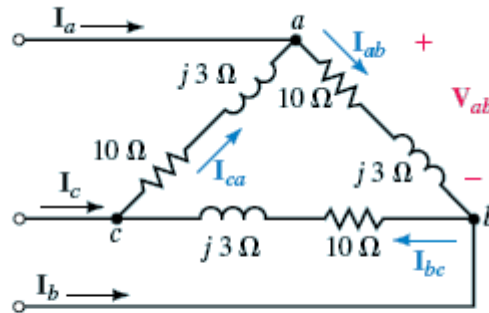**EXAMPLE 23-5** Suppose  $V_{ab} = 240 \text{ V} \angle 15^\circ$  for the circuit of Figure 23-13.

- Determine the phase currents.
- Determine the line currents.
- Sketch the phasor diagram.



**EWB** FIGURE 23-13

**Solution**

a.  $I_{ab} = \frac{V_{ab}}{Z_{ab}} = \frac{240 \angle 15^\circ}{10 + j3} = 23.0 \text{ A} \angle -1.70^\circ$

Thus,


$$I_{bc} = 23.0 \text{ A} \angle -121.7^\circ \quad \text{and} \quad I_{ca} = 23.0 \text{ A} \angle 118.3^\circ$$

b.  $I_a = \sqrt{3} I_{ab} \angle -30^\circ = 39.8 \text{ A} \angle -31.7^\circ$

Thus,

$$I_b = 39.8 \text{ A} \angle -151.7^\circ \quad \text{and} \quad I_c = 39.8 \text{ A} \angle 88.3^\circ$$

- c. Phasors are shown in Figure 23-14.

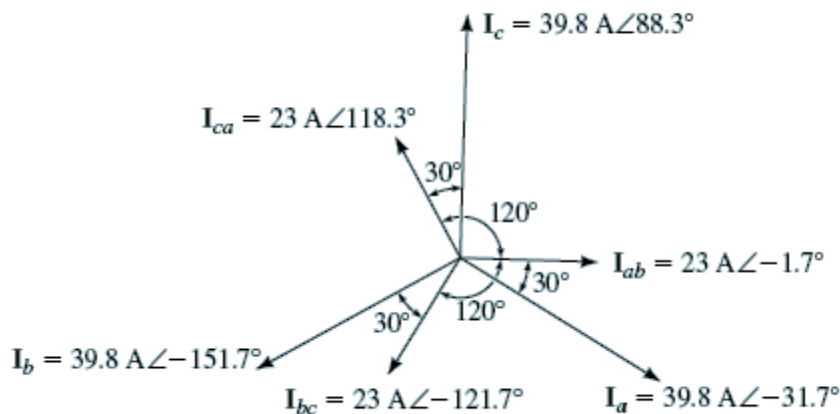

**FIGURE 23-14**

**EXAMPLE 23-12** Determine per phase and total power (active, reactive, and apparent) for Figure 23-25. Use  $V_\phi = 207.8$  V in order to compare results.

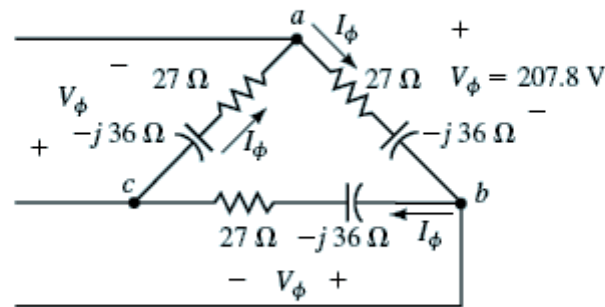


FIGURE 23-25

**Solution**

$$Z_\phi = 27 - j36 = 45 \Omega \angle -53.13^\circ, \text{ so } \theta_\phi = -53.13^\circ$$

$$V_\phi = 207.8 \text{ V} \text{ and } I_\phi = V_\phi / Z_\phi = 207.8 \text{ V} / 45 \Omega = 4.62 \text{ A}$$

$$P_\phi = V_\phi I_\phi \cos \theta_\phi = (207.8)(4.62) \cos(-53.13^\circ) = 576 \text{ W}$$

$$Q_\phi = V_\phi I_\phi \sin \theta_\phi = (207.8)(4.62) \sin(-53.13^\circ) = -768 \text{ VAR} \\ = 768 \text{ VAR (cap.)}$$

$$S_\phi = V_\phi I_\phi = (207.8)(4.62) = 960 \text{ VA}$$

$$P_T = 3P_\phi = 3(576) = 1728 \text{ W}$$

$$Q_T = 3Q_\phi = 3(768) = 2304 \text{ VAR (cap.)}$$

$$S_T = 3S_\phi = 3(960) = 2880 \text{ VA}$$

Note that the results here are the same as for Example 23-11. This is to be expected since the load of Figure 23-23 is the Y equivalent of the  $\Delta$  load of Figure 23-25.